

EGR 234 – Digital Logic Design
Lab 10:
Digital Clock Using Counters and VHDL

Lab Report by: Christopher Parisi
Lab Partner: No Partner
December 10, 2010

Exercise 1

VHDL Code for cntr_mod10

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

-----
entity cntr_mod10 is
port( Clear: in std_logic;
      Clock: in std_logic;
      Enable: in std_logic;
      Q: out std_logic_vector(3 downto 0);
      Nine: out std_logic );
end entity cntr_mod10;
```

```
-----
architecture cntr_mod10_arch of cntr_mod10 is
```

```
component cntr_reg is
port(  Clear: in std_logic;
        Clock: in std_logic;
        Enable: in std_logic;
        Load: in std_logic;
        D: in std_logic_vector(3 downto 0);
        Q: out std_logic_vector(3 downto 0) );
end component cntr_reg;
```

```
signal Load: std_logic;
signal Q_tmp: std_logic_vector(3 downto 0);
```


```
begin
```

```
Load <= Q_tmp(3) and Q_tmp(0);
cntr_reg1: cntr_reg
  port map ( Clear => Clear, Clock => Clock,
             Enable => Enable, Load => Load, D => "0000", Q => Q_tmp );

Q <= Q_tmp;
Nine <= Load;
```

```
end architecture cntr_mod10_arch;
```

Functional Waveform for cntr_mod10

 

Exercise 2

VHDL Code for one_sec_pulse.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```
entity one_sec_pulse is
port( Clock: in std_logic;
      Clear: in std_logic;
      Pulse: out std_logic );
end entity one_sec_pulse;
```

architecture one_sec_pulse_arch of one_sec_pulse is

```
component cntr_mod10 is
port( Clear: in std_logic;
      Clock: in std_logic;
      Enable: in std_logic;
      Q: out std_logic_vector(3 downto 0);
      Nine: out std_logic );
end component cntr_mod10;
```

```
component cntr_mod5 is
port( Clear: in std_logic;
      Clock: in std_logic;
      Enable: in std_logic;
      Q: out std_logic_vector(3 downto 0);
      Four: out std_logic );
end component cntr_mod5;
```

```

signal Four8, Nine7, Nine6, Nine5, Nine4, Nine3, Nine2, Nine1: std_logic;
signal Enable8, Enable7, Enable6, Enable5, Enable4, Enable3, Enable2: std_logic;
signal Q_tmp8, Q_tmp7, Q_tmp6, Q_tmp5, Q_tmp4, Q_tmp3, Q_tmp2, Q_tmp1:
std_logic_vector(3 downto 0);

begin

cntr_mod10_1: cntr_mod10
    port map ( Clear => Clear, Clock => Clock, Enable => '1',
               Q => Q_tmp1, Nine => Nine1 );

Enable2 <= Nine1;

cntr_mod10_2: cntr_mod10
    port map ( Clear => Clear, Clock => Clock, Enable => Enable2,
               Q => Q_tmp2, Nine => Nine2 );

Enable3 <= Nine2 and Nine1;

cntr_mod10_3: cntr_mod10
    port map ( Clear => Clear, Clock => Clock, Enable => Enable3,
               Q => Q_tmp3, Nine => Nine3 );

Enable4 <= Nine3 and Nine2 and Nine1;

cntr_mod10_4: cntr_mod10
    port map ( Clear => Clear, Clock => Clock, Enable => Enable4,
               Q => Q_tmp4, Nine => Nine4 );

Enable5 <= Nine4 and Nine3 and Nine2 and Nine1;

cntr_mod10_5: cntr_mod10
    port map ( Clear => Clear, Clock => Clock, Enable => Enable5,
               Q => Q_tmp5, Nine => Nine5 );

Enable6 <= Nine5 and Nine4 and Nine3 and Nine2 and Nine1;

cntr_mod10_6: cntr_mod10
    port map ( Clear => Clear, Clock => Clock, Enable => Enable6,
               Q => Q_tmp6, Nine => Nine6 );

Enable7 <= Nine6 and Nine5 and Nine4 and Nine3 and Nine2 and Nine1;

cntr_mod10_7: cntr_mod10
    port map ( Clear => Clear, Clock => Clock, Enable => Enable7,
               Q => Q_tmp7, Nine => Nine7 );

```

```

        Q => Q_tmp7, Nine => Nine7 );
Enable8 <= Nine7 and Nine6 and Nine5 and Nine4 and Nine3 and Nine2 and Nine1;

cntr_mod5_8: cntr_mod5
    port map ( Clear => Clear, Clock => Clock, Enable => Enable8,
                Q => Q_tmp8, Four => Four8 );

Pulse <= Four8 and Nine7 and Nine6 and Nine5 and Nine4 and Nine3 and Nine2 and Nine1;

end architecture one_sec_pulse_arch;

```

Exercise 3

VHDL Code for cntr_mod6

```

library ieee ;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
-----
```

```

entity cntr_mod6 is
port( Clear: in std_logic;
      Clock: in std_logic;
      Enable: in std_logic;
      Q: out std_logic_vector(3 downto 0);
      Five: out std_logic );
end entity cntr_mod6;
-----
```

```
architecture cntr_mod6_arch of cntr_mod6 is
```

```

component cntr_reg is
port(  Clear: in std_logic;
        Clock: in std_logic;
        Enable: in std_logic;
        Load: in std_logic;
        D: in std_logic_vector(3 downto 0);
        Q: out std_logic_vector(3 downto 0) );
end component cntr_reg;
```

```
signal Load: std_logic;
```

```

signal Q_tmp: std_logic_vector(3 downto 0);

begin


Load <= Q_tmp(2) and Q_tmp(1);
cntr_reg1: cntr_reg
    port map ( Clear => Clear, Clock => Clock,
    Enable => Enable, Load => Load, D => "0000", Q => Q_tmp );

Q <= Q_tmp;
Five <= Load;

end architecture cntr_mod6_arch;

```

Functional Waveform for cntr_mod6

 

VHDL Code for Digital Clock

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

```

```

entity Digital_Clock is
port( Clock: in std_logic;
      Clear: in std_logic;
      SecondOut0: out std_logic_vector(6 downto 0);
      SecondOut1: out std_logic_vector(6 downto 0);
      MinuteOut0: out std_logic_vector(6 downto 0);
      MinuteOut1: out std_logic_vector(6 downto 0));
end entity Digital_Clock;

```

```

architecture Digital_Clock_arch of Digital_Clock is

```

```

component cntr_mod10 is
port( Clear: in std_logic;

```

```

        Clock: in std_logic;
Enable: in std_logic;
        Q: out std_logic_vector(3 downto 0);
        Nine: out std_logic );
end component cntr_mod10;

component cntr_mod6 is
port( Clear: in std_logic;
Clock: in std_logic;
Enable: in std_logic;
        Q: out std_logic_vector(3 downto 0);
        Five: out std_logic );
end component cntr_mod6;

component one_sec_pulse is
port( Clear: in std_logic;
Clock: in std_logic;
Pulse: out std_logic );
end component one_sec_pulse;

component hex7seg is
port (hex : in std_logic_vector(3 downto 0);
      seg : out std_logic_vector(6 downto 0));
end component hex7seg;

signal Pulse0, Five4, Nine3, Five2, Nine1: std_logic;
signal Enable4, Enable3, Enable2, Enable1: std_logic;
signal Q_tmp4, Q_tmp3, Q_tmp2, Q_tmp1: std_logic_vector(3 downto 0);
signal Second0, Second1, Minute0, Minute1: std_logic_vector(6 downto 0);

begin

    One_sec_pulse_0: one_sec_pulse
        port map ( Clear => Clear, Clock => Clock, Pulse => Pulse0 );

    Enable1 <= Pulse0;

    cntr_mod10_1: cntr_mod10
        port map ( Clear => Clear, Clock => Clock, Enable => Enable1,
Q => Q_tmp1, Nine => Nine1 );

    Enable2 <= Nine1;

    cntr_mod6_2: cntr_mod6
        port map ( Clear => Clear, Clock => Clock, Enable => Enable2,
Q => Q_tmp2, Five => Five2);

```

```

Enable3 <= Nine1 and Five2;

cntr_mod10_3: cntr_mod10
    port map ( Clear => Clear, Clock => Clock, Enable => Enable3,
                Q => Q_tmp3, Nine => Nine3 );

Enable4 <= Nine1 and Five2 and Nine3;

cntr_mod6_4: cntr_mod6
    port map ( Clear => Clear, Clock => Clock, Enable => Enable4,
                Q => Q_tmp4, Five => Five4 );

hex7seg_5: hex7seg
    port map (hex => Q_tmp1, seg => Second0);

hex7seg_6: hex7seg
    port map (hex => Q_tmp2, seg => Second1);

hex7seg_7: hex7seg
    port map (hex => Q_tmp3, seg => Minute0);

hex7seg_8: hex7seg
    port map (hex => Q_tmp4, seg => Minute1);

SecondOut0 <= Second0;
SecondOut1 <= Second1;
MinuteOut0 <= Minute0;
MinuteOut1 <= Minute1;

end architecture Digital_Clock_arch;

```