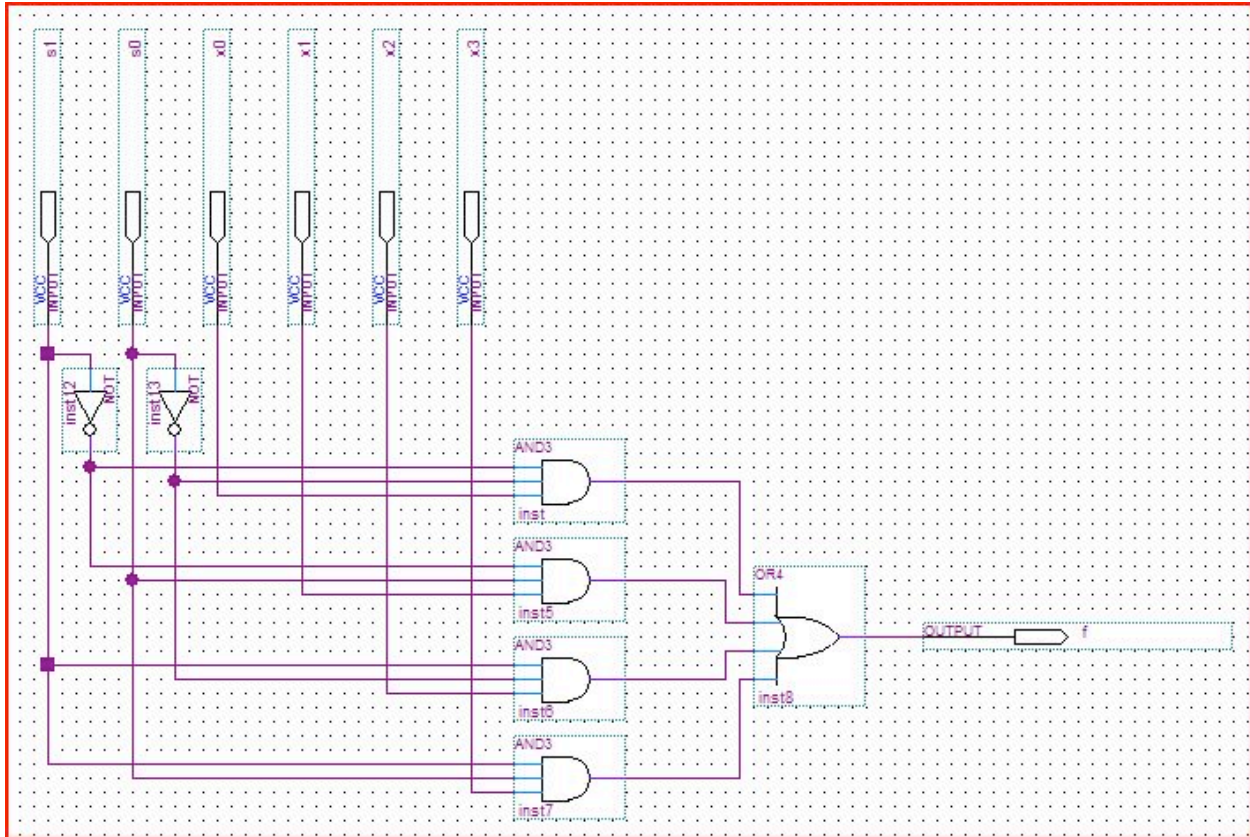


EGR 234 – Digital Logic Design
Lab 5:
Digital Logic Circuit Design Using the DE2
Board

Lab Report by: Christopher Parisi
Lab Partner: No Partner
October 8, 2010

Exercise


Circuit Schematic for 4-1 MUX



Functional Waveform



Timing Waveform

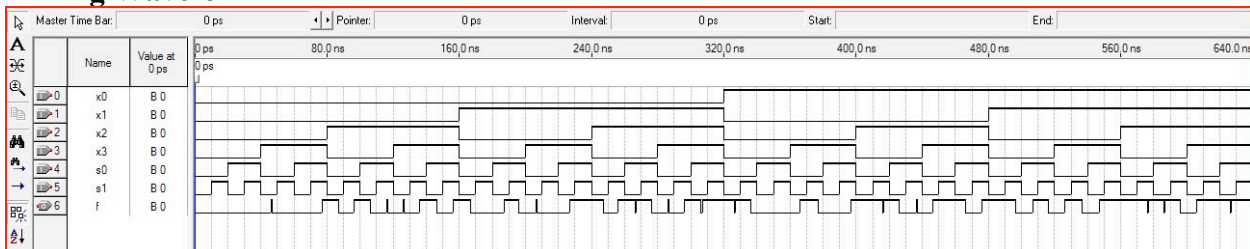

Truth Table

X0	X1	X2	X3	S0	S1	f
0	0	0	0	0	0	0
0	0	0	0	0	1	0
0	0	0	0	1	0	0
0	0	0	0	1	1	0
0	0	0	1	0	0	0
0	0	0	1	0	1	0
0	0	0	1	1	0	0
0	0	0	1	1	1	1
0	0	1	0	0	0	0
0	0	1	0	0	1	1
0	0	1	0	1	0	0
0	0	1	0	1	1	0
0	0	1	1	0	0	0
0	0	1	1	0	1	1
0	0	1	1	1	0	0
0	0	1	1	1	1	1
0	1	0	0	0	0	0
0	1	0	0	0	1	0
0	1	0	0	1	0	1
0	1	0	0	1	1	0
0	1	0	1	0	0	0
0	1	0	1	0	1	0
0	1	0	1	1	0	1
0	1	0	1	1	1	1
0	1	1	0	0	0	0
0	1	1	0	0	1	1
0	1	1	0	1	0	1
0	1	1	0	1	1	0
0	1	1	1	0	0	0
0	1	1	1	0	1	1
0	1	1	1	1	0	1
0	1	1	1	1	1	1
1	0	0	0	0	0	1
1	0	0	0	0	1	0
1	0	0	0	1	0	0
1	0	0	0	1	1	0
1	0	0	1	0	0	1
1	0	0	1	0	1	0
1	0	0	1	1	0	0
1	0	0	1	1	1	1
1	0	1	0	0	0	1
1	0	1	0	0	1	1

1	0	1	0	1	0	0
1	0	1	0	1	1	0
1	0	1	1	0	0	1
1	0	1	1	0	1	1
1	0	1	1	1	0	0
1	0	1	1	1	1	1
1	1	0	0	0	0	1
1	1	0	0	0	1	0
1	1	0	0	1	0	1
1	1	0	0	1	1	0
1	1	0	1	0	0	1
1	1	0	1	0	1	0
1	1	0	1	1	0	1
1	1	0	1	1	1	1
1	1	1	0	0	0	1
1	1	1	0	0	1	1
1	1	1	0	1	0	1
1	1	1	0	1	1	0
1	1	1	1	0	0	1
1	1	1	1	0	1	1
1	1	1	1	1	0	1
1	1	1	1	1	1	1

The truth table shows the 64 different outputs of the 4-1 MUX. This truth table matches up to the results of the waveform. The results also match up to the DE2 Board LED's. This shows the Quartus II program is able to accurately represent a 4-1 MUX and upload the logical circuit to the Cyclone II chip.