

EGR 234 – Digital Logic Design
Lab 7:
Modular Approach for Adder Implementation


Lab Report by: Christopher Parisi
Lab Partner: No Partner
October 15, 2010

Exercise 1


VHDL code for 1-bit full adder

```
-----  
-- 1-bit full adder  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
  
entity fa is  
port (x, y, cin : in std_logic;  
      s, cout : out std_logic);  
end fa;  
  
architecture fa_arch of fa is  
    signal input : std_logic_vector (2 downto 0);  
    signal output : std_logic_vector (1 downto 0);  
begin  
    input <= cin & x & y;  
  
    with input select  
        output <= "00" when "000",  
                "10" when "001",  
                "10" when "010",  
                "01" when "011",  
                "10" when "100",  
                "01" when "101",  
                "01" when "110",  
                "11" when "111",  
                "00" when others;  
  
        s <= output(1);  
        cout <= output(0);  
end fa_arch;
```

Functional Simulation Waveform

 

Timing Simulation Waveform

 


Truth Table

cin	x	y	s	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


This truth table coincides with the waveform and shows the functionality of the 1-bit adder.

Exercise 2

Schematic for 4-bit adder

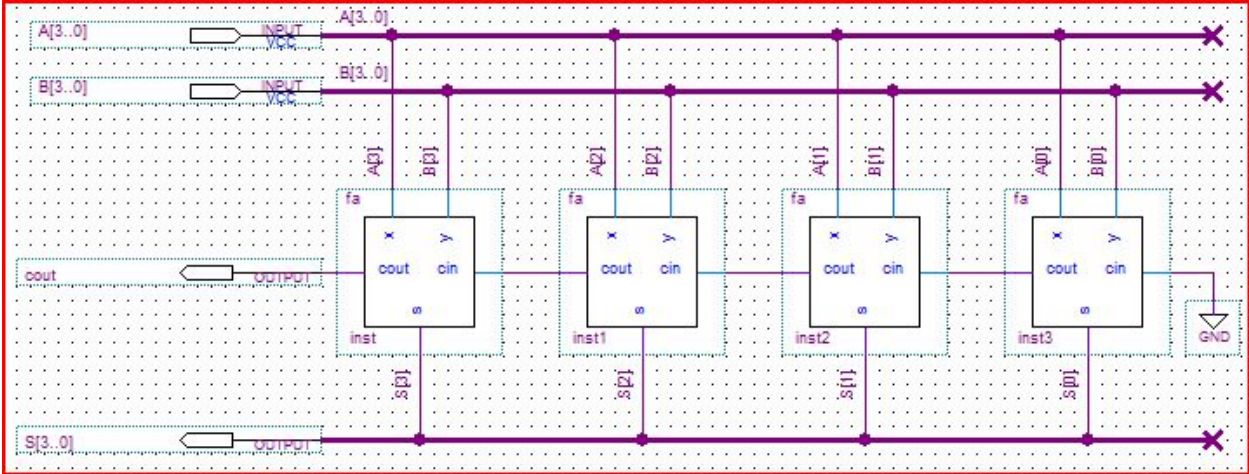


Function Simulation Waveform

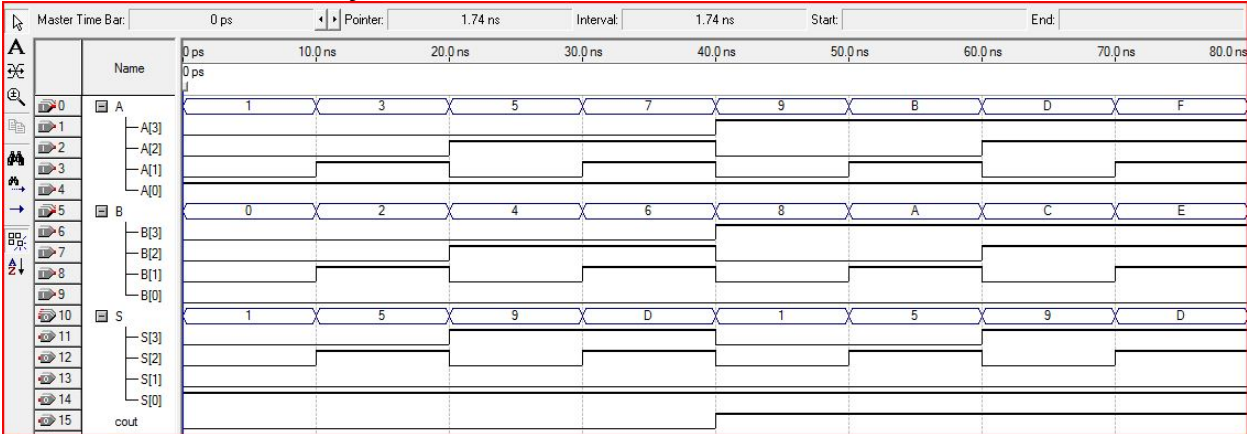

Exercise 3

Schematic for completed adder

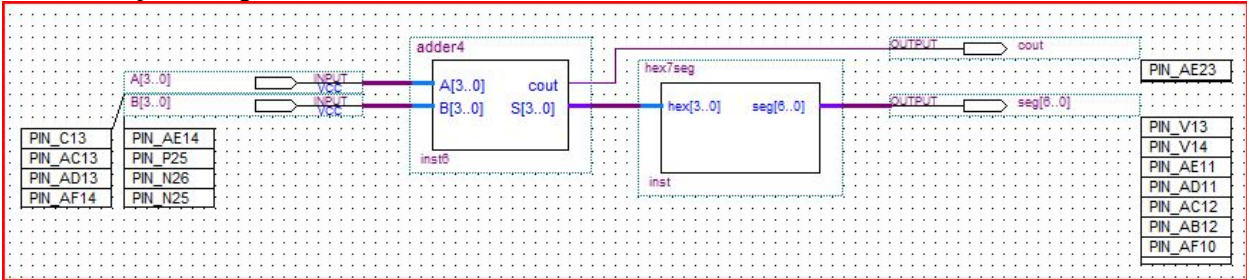

This schematic was then programmed into the DE2 board and tested. The results match up with the waveform from Exercise 2. This shows that the Modular Approach is capable of solving many problems. The modular approach is easy and organizes the problem making it easier to read and implement.